

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем»
на тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №21

Виконав:
ст. гр. КІ-201
Патрило Ю.А.
Прийняв:
ст. викладач
каф. ЕОМ
Козак Н. Б.

Львів 2024

Мета роботи: На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Виконання роботи:

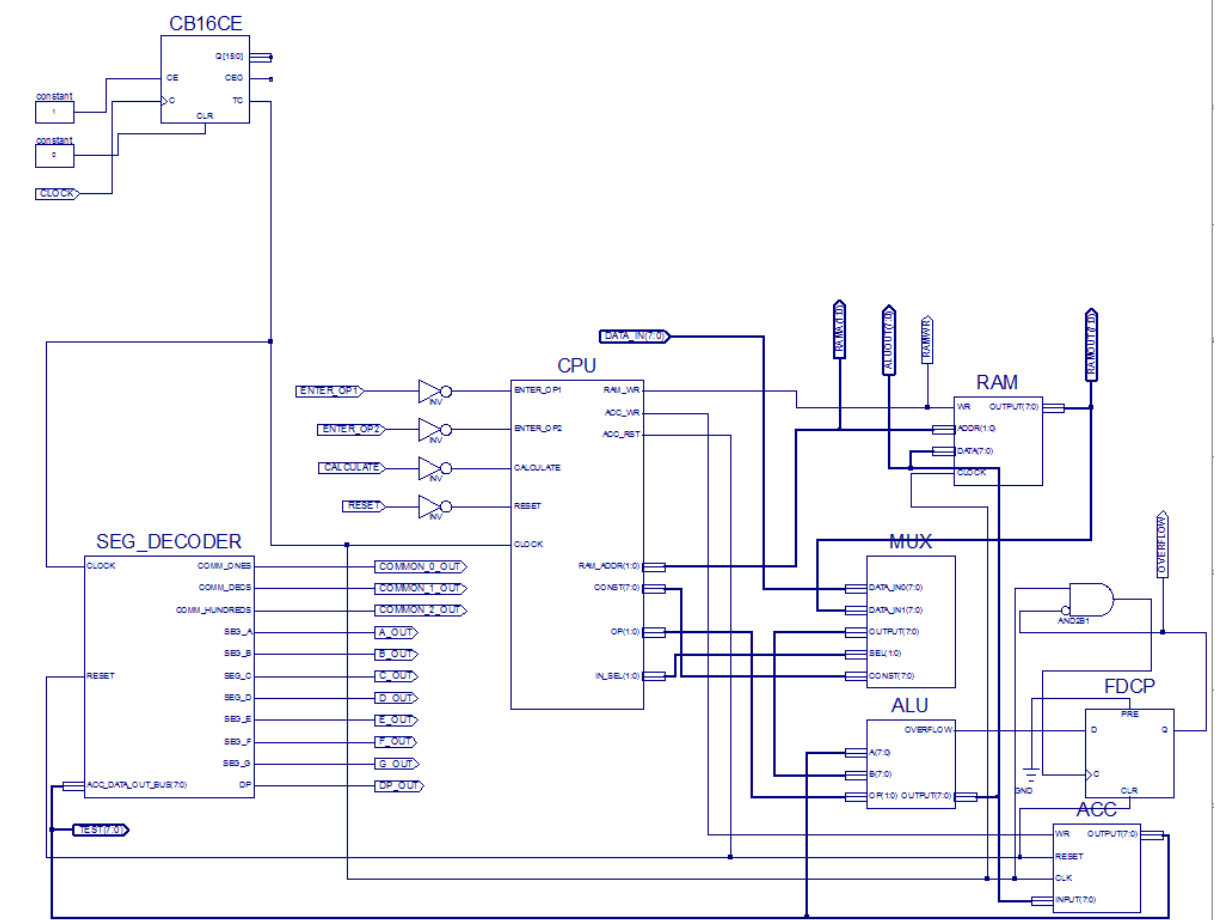


Рис. 1 – Top Level

Файл ACC.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ACC is
    Port ( WR : in STD_LOGIC;
          RESET : in STD_LOGIC;
          CLK : in STD_LOGIC;
          INPUT : in STD_LOGIC_VECTOR (7 downto 0);
          OUTPUT : out STD_LOGIC_VECTOR (7 downto 0));
end ACC;

architecture ACC_arch of ACC is
    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
```

```

begin
  process (CLK)
  begin
    if rising_edge(CLK) then
      if RESET = '1' then
        DATA <= (others => '0');
      elsif WR = '1' then
        DATA <= INPUT;
      end if;
    end if;
  end process;

  OUTPUT <= DATA;

end ACC_arch;

```

Файл ALU.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ALU is
  Port ( A : in  STD_LOGIC_VECTOR(7 downto 0);
        B : in  STD_LOGIC_VECTOR(7 downto 0);
        OP : in  STD_LOGIC_VECTOR(1 downto 0);
        OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
        OVERFLOW: out STD_LOGIC);
end ALU;

architecture ALU_Behavioral of ALU is
  signal ALUR: STD_LOGIC_VECTOR(15 downto 0) := (others => '0');
  signal Carry: STD_LOGIC := '0';
begin
  process(A, B, OP)
  begin
    case (OP) is

```

```

        when "01" => ALUR <= ("00000000" & A) +
("00000000" & B);
        when "10" => ALUR <= ("00000000" & A) +
("11111111" & not B) + "0000000000000001";
        when "11" => ALUR <= ("00000000" & A) or
("00000000" & B);
        when others => ALUR <= ("00000000" & B);
    end case;
end process;
OUTPUT <= ALUR(7 downto 0);
OVERFLOW <= ALUR(8) OR ALUR(9) OR ALUR(10) OR
ALUR(11) OR ALUR(12) OR ALUR(13) OR ALUR(14) OR ALUR(15);
end ALU_Behavioral;

```

```

Файл CPU.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CPU is
    port( ENTER_OP1 : IN STD_LOGIC;
          ENTER_OP2 : IN STD_LOGIC;
          CALCULATE : IN STD_LOGIC;
          RESET : IN STD_LOGIC;
          CLOCK : IN STD_LOGIC;
          RAM_WR : OUT STD_LOGIC;
          RAM_ADDR : OUT STD_LOGIC_VECTOR(1
DOWNTO 0);
          CONST : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
          ACC_WR : OUT STD_LOGIC;
          ACC_RST : OUT STD_LOGIC;
          IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
          OP : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
end CPU;

architecture CPU_arch of CPU is

type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2,
RUN_CALC0, RUN_CALC1, RUN_CALC2, RUN_CALC3, RUN_CALC4,
FINISH);
signal CUR_STATE : STATE_TYPE;
signal NEXT_STATE : STATE_TYPE;

```

```

begin
    SYNC_PROC: process (CLOCK)
    begin
        if (rising_edge(CLOCK)) then
            if (RESET = '1') then
                CUR_STATE <= RST;
            else
                CUR_STATE <= NEXT_STATE;
            end if;
        end if;
    end process;

    NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1,
ENTER_OP2, CALCULATE)
    begin
        NEXT_STATE <= CUR_STATE;

        case(CUR_STATE) is
            when RST =>
                NEXT_STATE <= IDLE;
            when IDLE      =>
                if (ENTER_OP1 = '1') then
                    NEXT_STATE <= LOAD_OP1;
                elsif (ENTER_OP2 = '1') then
                    NEXT_STATE <= LOAD_OP2;
                elsif (CALCULATE = '1') then
                    NEXT_STATE <= RUN_CALC0;
                else
                    NEXT_STATE <= IDLE;
                end if;
            when LOAD_OP1      =>
                NEXT_STATE <= IDLE;
            when LOAD_OP2      =>
                NEXT_STATE <= IDLE;
            when RUN_CALC0 =>
                NEXT_STATE <= RUN_CALC1;
            when RUN_CALC1 =>
                NEXT_STATE <= RUN_CALC2;
            when RUN_CALC2 =>
                NEXT_STATE <= RUN_CALC3;
            when RUN_CALC3 =>

```

```

        NEXT_STATE <= RUN_CALC4;
    when RUN_CALC4 =>
        NEXT_STATE <= FINISH;
    when FINISH =>
        NEXT_STATE <= FINISH;
    when others =>
        NEXT_STATE <= IDLE;
    end case;
end process;

```

```

OUTPUT_DECODE: process (CUR_STATE)
begin

```

```

    case (CUR_STATE) is
        when RST =>
            RAM_WR <= '0';
            RAM_ADDR <= "00";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when LOAD_OP1 =>
            RAM_WR <= '1';
            RAM_ADDR <= "00";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when LOAD_OP2 =>
            RAM_WR <= '1';
            RAM_ADDR <= "01";
            CONST <= "00000000";
            ACC_WR <= '0';
            ACC_RST <= '1';
            IN_SEL <= "00";
            OP <= "00";
        when RUN_CALC0 =>
            RAM_WR <= '0';
            RAM_ADDR <= "01";
            CONST <= "00000000";
            ACC_WR <= '1';
            ACC_RST <= '0';

```

```

        IN_SEL <= "01";
        OP <= "00";
when RUN_CALC1 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000100";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "11";
when RUN_CALC2 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "01";
when RUN_CALC3 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00001010";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "01";
when RUN_CALC4 =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000010";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "10";
when IDLE =>
    RAM_WR <= '0';
    RAM_ADDR <= "00";
    CONST <= "00000000";
    ACC_WR <= '0';
    ACC_RST <= '0';
    IN_SEL <= "00";
    OP <= "00";
when others =>

```

```

        RAM_WR <= '0';
        RAM_ADDR <= "00";
        CONST <= "00000000";
        ACC_WR <= '0';
        ACC_RST <= '0';
        IN_SEL <= "00";
        OP <= "00";

    end case;
end process;
end CPU_arch;

```

Файл MUX.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX is
    PORT(
        SEL: in STD_LOGIC_VECTOR(1 downto 0);
        CONST: in STD_LOGIC_VECTOR(7 downto 0);
        --CONST1: in STD_LOGIC_VECTOR()
        DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);
        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
    );
end MUX;

architecture Behavioral of MUX is
begin
    process (SEL, DATA_IN0, DATA_IN1, CONST)
    begin
        if (SEL = "00") then
            OUTPUT <= DATA_IN0;
        elsif (SEL = "01") then
            OUTPUT <= DATA_IN1;
        else
            OUTPUT <= CONST;
        end if;
    end process;
end Behavioral;

```



```

Файл RAM.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity RAM is
    port(
        WR : IN STD_LOGIC;
        ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        CLOCK: IN STD_LOGIC;
        OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
    );
end RAM;

architecture RAM_arch of RAM is
    type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7
downto 0);
    signal UNIT : ram_type;

begin
    process(ADDR, CLOCK, UNIT)
    begin
        if(rising_edge(CLOCK)) then
            if (WR = '1') then
                UNIT(conv_integer(ADDR)) <= DATA;
            end if;
        end if;
        OUTPUT <= UNIT(conv_integer(ADDR));
    end process;
end RAM_arch;

```

```

Файл SEG_DECODER.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity SEG_DECODER is

```

```

port( CLOCK : IN STD_LOGIC;
      RESET : IN STD_LOGIC;
      ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7
DOWNTO 0);
      COMM_ONES          : OUT STD_LOGIC;
      COMM_DECS          : OUT STD_LOGIC;
      COMM_HUNDREDS      : OUT STD_LOGIC;
      SEG_A              : OUT STD_LOGIC;
      SEG_B              : OUT STD_LOGIC;
      SEG_C              : OUT STD_LOGIC;
      SEG_D              : OUT STD_LOGIC;
      SEG_E              : OUT STD_LOGIC;
      SEG_F              : OUT STD_LOGIC;
      SEG_G              : OUT STD_LOGIC;
      DP                 : OUT STD_LOGIC);
end SEG_DECODER;

```

architecture Behavioral of SEG_DECODER is

```

    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) :=
"0000";

```

begin

```

    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
    variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
    variable bcd     : STD_LOGIC_VECTOR(11 downto 0) ;

```

begin

```

    bcd      := (others => '0') ;
    hex_src   := ACC_DATA_OUT_BUS;

```

```

    for i in hex_src'range loop

```

```

        if bcd(3 downto 0) > "0100" then
            bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;

```

```

        end if ;

```

```

        if bcd(7 downto 4) > "0100" then
            bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;

```

```

        end if ;

```

```

        if bcd(11 downto 8) > "0100" then
            bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;

```

```

        end if ;

```

```

        bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new
entry
        hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; --
shift src + pad with 0
    end loop ;

HONDREDS_BUS    <= bcd (11 downto 8);
DECS_BUS        <= bcd (7 downto 4);
ONES_BUS        <= bcd (3 downto 0);

end process BIN_TO_BCD;

INDICATE : process(CLOCK)
    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

    variable CUR_DIGIT    : DIGIT_TYPE := ONES;
    variable DIGIT_VAL    : STD_LOGIC_VECTOR(3 downto 0)
:= "0000";
    variable DIGIT_CTRL   : STD_LOGIC_VECTOR(6 downto 0)
:= "0000000";
    variable COMMONS_CTRL : STD_LOGIC_VECTOR(2
downto 0) := "000";

    begin
        if (rising_edge(CLOCK)) then
            if(RESET = '0') then
                case CUR_DIGIT is
                    when ONES =>
                        DIGIT_VAL := ONES_BUS;
                        CUR_DIGIT := DECS;
                        COMMONS_CTRL := "001";
                    when DECS =>
                        DIGIT_VAL := DECS_BUS;
                        CUR_DIGIT := HUNDREDS;
                        COMMONS_CTRL := "010";
                    when HUNDREDS =>
                        DIGIT_VAL :=
HONDREDS_BUS;

                        CUR_DIGIT := ONES;
                        COMMONS_CTRL := "100";
                    when others =>
                        DIGIT_VAL := ONES_BUS;
                        CUR_DIGIT := ONES;

```

```

COMMONS_CTRL := "000";
end case;

case DIGIT_VAL is      --abcdefg
    when "0000" => DIGIT_CTRL :=
"1111110";
    when "0001" => DIGIT_CTRL :=
"0110000";
    when "0010" => DIGIT_CTRL :=
"1101101";
    when "0011" => DIGIT_CTRL :=
"1111001";
    when "0100" => DIGIT_CTRL :=
"0110011";
    when "0101" => DIGIT_CTRL :=
"1011011";
    when "0110" => DIGIT_CTRL :=
"1011111";
    when "0111" => DIGIT_CTRL :=
"1110000";
    when "1000" => DIGIT_CTRL :=
"1111111";
    when "1001" => DIGIT_CTRL :=
"1111011";
    when others => DIGIT_CTRL :=
"0000000";

end case;
else
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";
end if;

COMM_ONES    <= not COMMONS_CTRL(0);
COMM_DECS    <= not COMMONS_CTRL(1);
COMM_HUNDREDS <= not
COMMONS_CTRL(2);

SEG_A <= not DIGIT_CTRL(6);
SEG_B <= not DIGIT_CTRL(5);
SEG_C <= not DIGIT_CTRL(4);
SEG_D <= not DIGIT_CTRL(3);
SEG_E <= not DIGIT_CTRL(2);

```

```
SEG_F <= not DIGIT_CTRL(1);
SEG_G <= not DIGIT_CTRL(0);
DP    <= '1';

    end if;
end process INDICATE;

end Behavioral;
```

 


Рис. 2 – Часова діаграма ACC

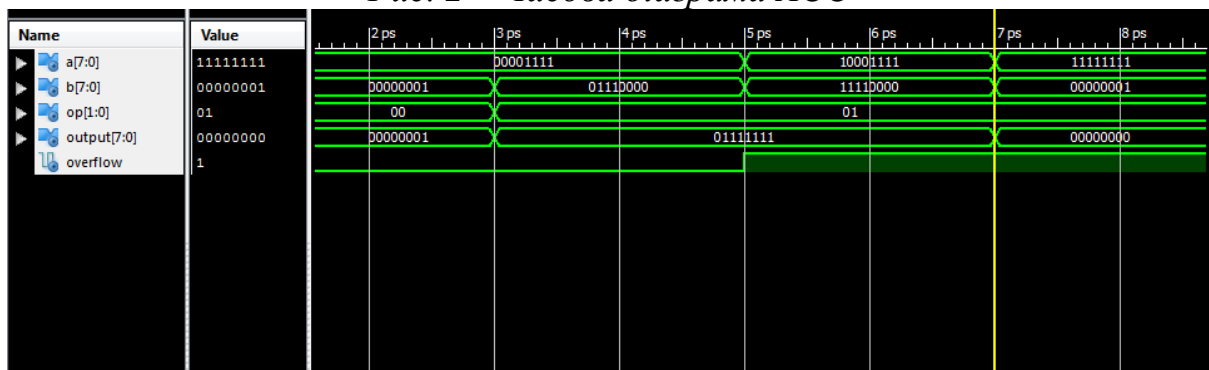


Рис. 3 – Часова діаграма ALU

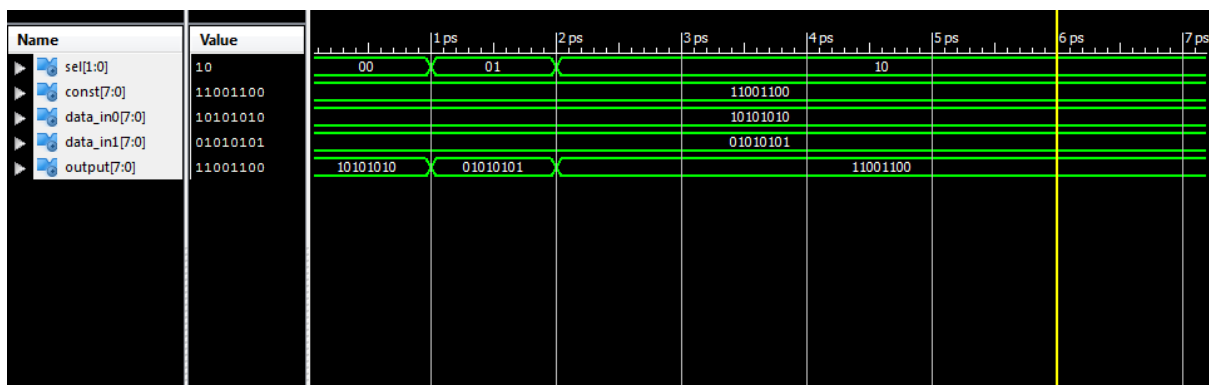


Рис. 4 – Часова діаграма MUX

 


Рис. 5 – Часова діаграма RAM

 


Рис 6. – Часова діаграма SEG_DECODER

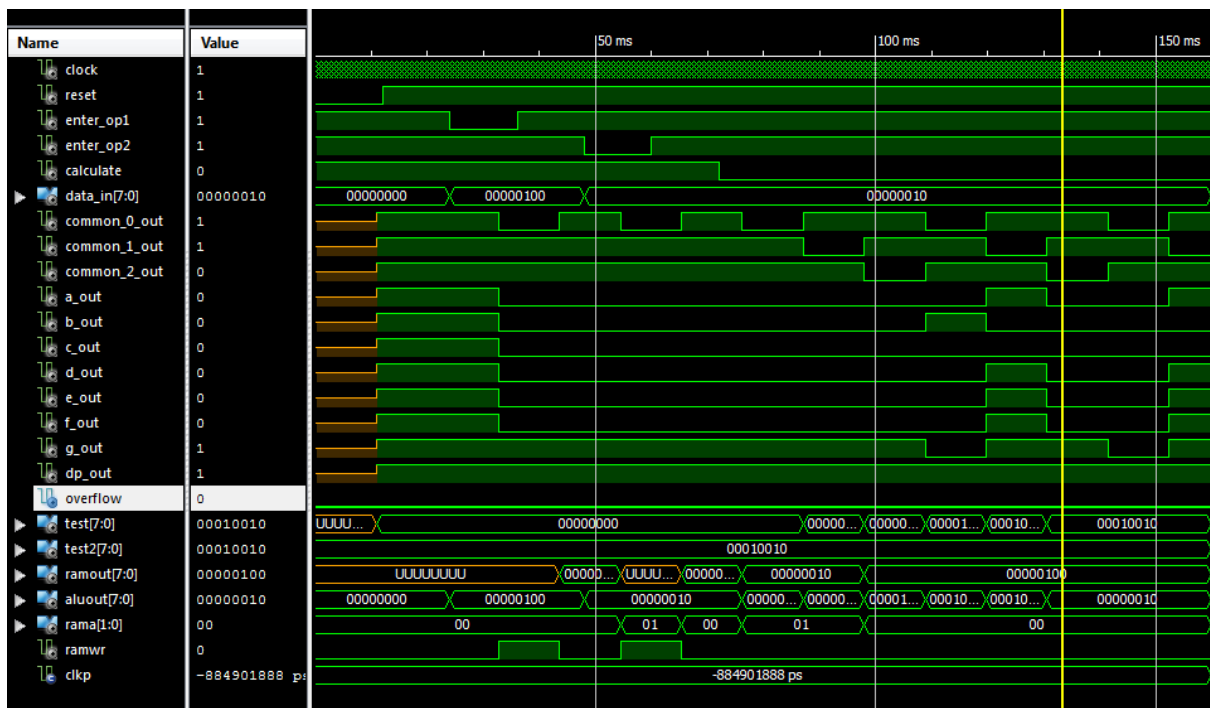


Рис 7. – Часова діаграма TopLevel

Файл TopLevelTest.vhd

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.numeric_std.ALL;

LIBRARY UNISIM;

USE UNISIM.Vcomponents.ALL;

ENTITY TopLevel_TopLevel_sch_tb IS

END TopLevel_TopLevel_sch_tb;

ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS

COMPONENT TopLevel

PORT(CLOCK : IN STD_LOGIC;

RESET : IN STD_LOGIC;

ENTER_OP1 : IN STD_LOGIC;

ENTER_OP2 : IN STD_LOGIC;

CALCULATE : IN STD_LOGIC;

DATA_IN : IN STD_LOGIC_VECTOR (7 DOWNT0 0);

COMMON_0_OUT : OUT STD_LOGIC;

COMMON_1_OUT : OUT STD_LOGIC;

COMMON_2_OUT : OUT STD_LOGIC;

TEST: OUT STD_LOGIC_VECTOR(7 downto 0);

A_OUT : OUT STD_LOGIC;

B_OUT : OUT STD_LOGIC;

C_OUT : OUT STD_LOGIC;

D_OUT : OUT STD_LOGIC;

E_OUT : OUT STD_LOGIC;

F_OUT : OUT STD_LOGIC;

G_OUT : OUT STD_LOGIC;

DP_OUT : OUT STD_LOGIC;

RAMOUT: OUT STD_LOGIC_VECTOR(7 downto 0);

ALUOUT: OUT STD_LOGIC_VECTOR(7 downto 0);

RAMA: OUT STD_LOGIC_VECTOR(1 downto 0);

RAMWR: OUT STD_LOGIC;

OVERFLOW : OUT STD_LOGIC);

END COMPONENT;

SIGNAL CLOCK : STD_LOGIC := '0';

SIGNAL RESET : STD_LOGIC;

SIGNAL ENTER_OP1 : STD_LOGIC;

SIGNAL ENTER_OP2 : STD_LOGIC;

SIGNAL CALCULATE : STD_LOGIC;

SIGNAL DATA_IN : STD_LOGIC_VECTOR (7 DOWNT0 0);

```

SIGNAL COMMON_0_OUT :    STD_LOGIC;
SIGNAL COMMON_1_OUT :    STD_LOGIC;
SIGNAL COMMON_2_OUT :    STD_LOGIC;
SIGNAL A_OUT:          STD_LOGIC;
SIGNAL B_OUT:          STD_LOGIC;
SIGNAL C_OUT:          STD_LOGIC;
SIGNAL D_OUT          :    STD_LOGIC;
SIGNAL E_OUT:          STD_LOGIC;
SIGNAL F_OUT:          STD_LOGIC;
SIGNAL G_OUT          :    STD_LOGIC;
SIGNAL DP_OUT          :    STD_LOGIC;
SIGNAL OVERFLOW :      STD_LOGIC;
    SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
    SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);
    signal RAMA: STD_LOGIC_VECTOR(1 downto 0);
    signal RAMWR: STD_LOGIC;

--    constant CLOCK_period : time := 166ns;
    constant CLKP: time := 12ms;--24ms;

```

BEGIN

```

    UUT: TopLevel PORT MAP(
        CLOCK => CLOCK,
        RESET => RESET,
        ENTER_OP1 => ENTER_OP1,
        ENTER_OP2 => ENTER_OP2,
        CALCULATE => CALCULATE,
        DATA_IN => DATA_IN,
        COMMON_0_OUT => COMMON_0_OUT,
        COMMON_1_OUT => COMMON_1_OUT,
        COMMON_2_OUT => COMMON_2_OUT,
        A_OUT => A_OUT,
        B_OUT => B_OUT,
        C_OUT => C_OUT,
        D_OUT => D_OUT,
        E_OUT => E_OUT,
        F_OUT => F_OUT,
        G_OUT => G_OUT,
        DP_OUT => DP_OUT,
        OVERFLOW => OVERFLOW,

```



```

        TEST => TEST,
        RAMOUT => RAMOUT,
        ALUOUT => ALUOUT,
        RAMA => RAMA,
        RAMWR => RAMWR
    );

    CLOCK_process: process
    begin
        CLOCK <= '0';
        wait for 83ns;
        CLOCK <= '1';
        wait for 83ns;
    end process;

-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    lp1: for i in 4 to 4 loop
        lp2: for j in 2 to 2 loop
            TEST2 <=
std_logic_vector(to_unsigned(to_integer(signed(std_logic_vector(to_unsigne
d(j, 8)) or std_logic_vector(to_unsigned(4, 8)))) + i + 10 - 2, 8));
            ENTER_OP1 <= '1';
            ENTER_OP2 <= '1';
            CALCULATE <= '1';
            DATA_IN <= (others => '0');
            RESET <= '0';
            wait for CLKP;
            RESET <= '1';
            wait for CLKP;
            DATA_IN <= std_logic_vector(to_unsigned(i, 8)); --
A
            ENTER_OP1 <= '0';
            wait for CLKP;
            ENTER_OP1 <= '1';
            wait for CLKP;
            DATA_IN <= std_logic_vector(to_unsigned(j, 8)); --
B
            ENTER_OP2 <= '0';
            wait for CLKP;
            ENTER_OP2 <= '1';
            wait for CLKP;

```

```

        CALCULATE <= '0'; -- START CALCULATION
        wait for CLKP* 7;
        assert TEST = TEST2 severity FAILURE;
        wait for CLKP;
    end loop;
end loop;

    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***

END;

```

 


Рис.8 – 7-сегментний індикатор

Переглянемо часову діаграму 7seg decoder.

Бачимо, що для вхідного числа $00001111(2) = 15(10)$

Ми отримуємо такі значення(якщо значення не вказане, вважаємо його за одиницю):

COMM_ONES = 0: A,C,D, F, G = 0, що відповідає числу 5

COMM_DECS = 0: B,C = 0, що відповідає числу 1

COMM_HUNDREDS = 0: A,B,C,D,E,F = 0, що відповідає числу 0

Отримуємо значення 015, що збігається з даним йому.

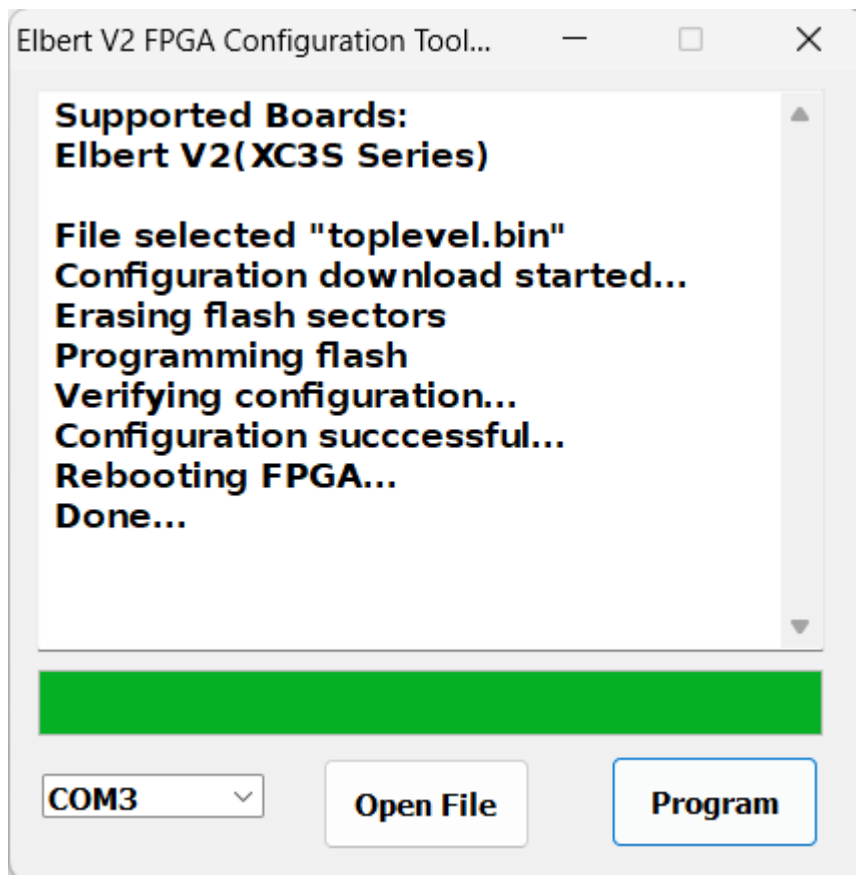


Рис.9 – Успішна прошивка

Висновок: Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.